
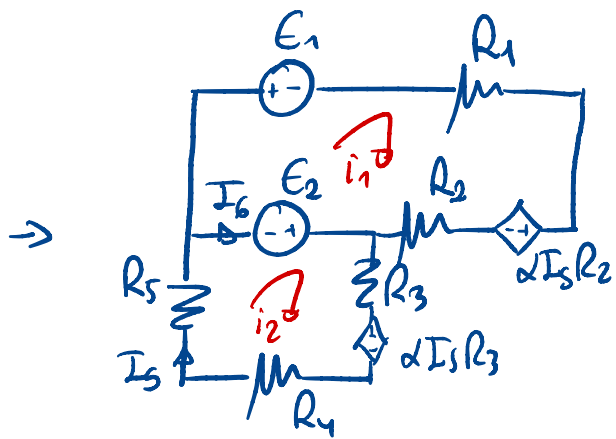


Problema 1 I_6 , mallas αI_6 βU_5

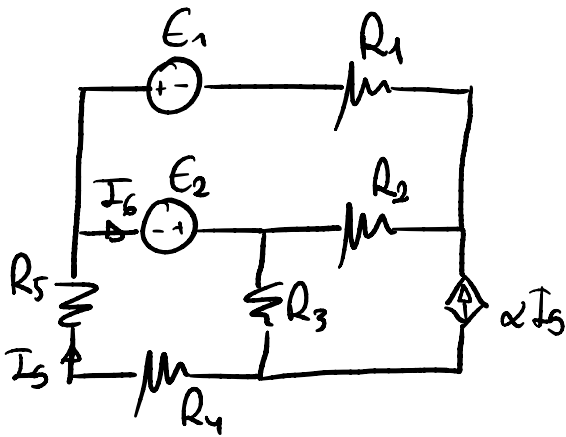

$$i_1 \quad -E_1 - \alpha I_5 R_2 - E_2 = i_1 (R_1 + R_2) \quad \overset{I_5 = i_2}{\rightarrow} -E_1 - E_2 = i_1 (R_1 + R_2) + i_2 \alpha R_2$$

$$i_2 \quad E_2 - \alpha I_5 R_3 = i_2 (R_3 + R_4 + R_5) \quad \overset{I_5 = i_2}{\rightarrow} E_2 = i_2 (R_3(1 + \alpha) + R_4 + R_5)$$

$$\hat{e}_s = Z_m \hat{i}_s \rightarrow \begin{pmatrix} -E_1 - E_2 \\ E_2 \end{pmatrix} = \begin{pmatrix} R_1 + R_2 & \alpha R_2 \\ 0 & R_3(1 + \alpha) + R_4 + R_5 \end{pmatrix} \begin{pmatrix} i_1 \\ i_2 \end{pmatrix}$$

$$i_1 = \frac{\begin{vmatrix} -(E_1 + E_2) & \alpha R_2 \\ E_2 & R_3(1 + \alpha) + R_4 + R_5 \end{vmatrix}}{\begin{vmatrix} R_1 + R_2 & \alpha R_2 \\ 0 & R_3(1 + \alpha) + R_4 + R_5 \end{vmatrix}} = \frac{-(E_1 + E_2)(R_3(1 + \alpha) + R_4 + R_5) - E_2 \alpha R_2}{(R_1 + R_2)(R_3(1 + \alpha) + R_4 + R_5)}$$


$$i_2 = \frac{\begin{vmatrix} R_1 + R_2 & -(E_1 + E_2) \\ 0 & E_2 \end{vmatrix}}{\begin{vmatrix} R_1 + R_2 & \alpha R_2 \\ 0 & R_3(1 + \alpha) + R_4 + R_5 \end{vmatrix}} = \frac{E_2(R_1 + R_2)}{(R_1 + R_2)(R_3(1 + \alpha) + R_4 + R_5)}$$

$$I_5 = i_1 + I_6 \rightarrow I_6 = I_5 - i_1 = i_2 - i_1 = \frac{E_2(R_1 + R_2) + (E_1 + E_2)(R_3(1 + \alpha) + R_4 + R_5) + E_2 \alpha R_2}{(R_1 + R_2)(R_3(1 + \alpha) + R_4 + R_5)}$$


Problema 1. Añadido 1 $\diamond \alpha I_6$

$$i_1 = I_6 + i_2$$

$$I_6 = i_1 - i_2$$

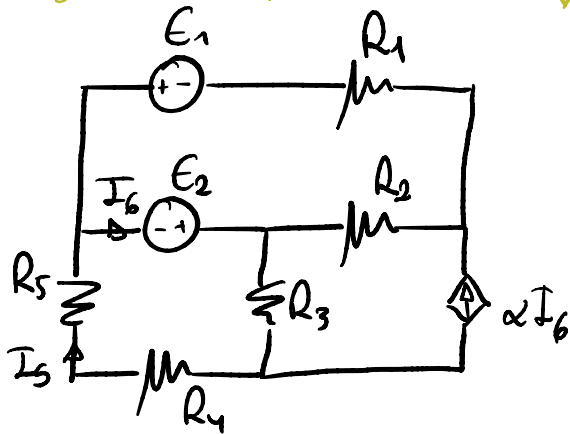

\rightarrow

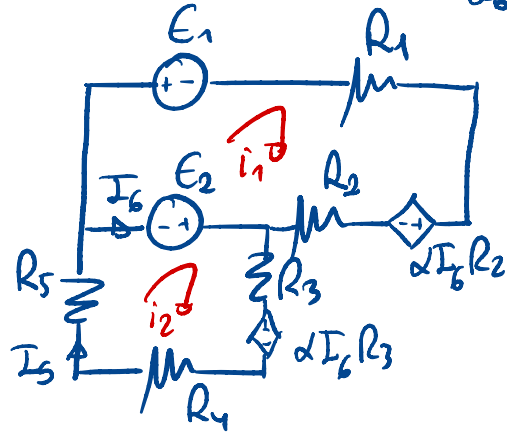


$$i_1 \text{ loop: } -E_1 - \alpha I_6 R_2 - E_2 = i_1 (R_1 + R_2) \quad I_6 = i_1 - i_2 \rightarrow -E_1 - E_2 = i_1 (R_1 + R_2 (1 + \alpha)) - i_2 \alpha R_2$$


$$i_2 \text{ loop: } E_2 - \alpha I_6 R_3 = i_2 (R_3 + R_4 + R_5) \quad I_6 = i_1 - i_2 \rightarrow E_2 = i_2 (R_3 (1 + \alpha) + R_4 + R_5) + i_1 \alpha R_3$$

$$\hat{e}_8 = Z_m \hat{i}_8 \rightarrow \begin{pmatrix} -(E_1 + E_2) \\ E_2 \end{pmatrix} = \begin{pmatrix} R_1 + R_2 (1 + \alpha) & -\alpha R_2 \\ \alpha R_3 & R_3 (1 + \alpha) + R_4 + R_5 \end{pmatrix} \begin{pmatrix} i_1 \\ i_2 \end{pmatrix}$$

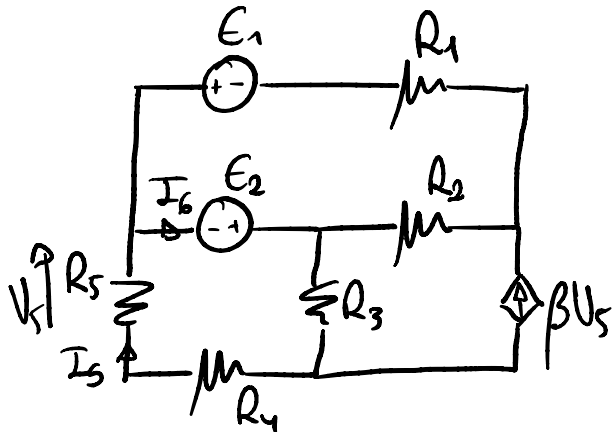Problema 1. Añadido 2 $\diamond \beta U_5$





\rightarrow

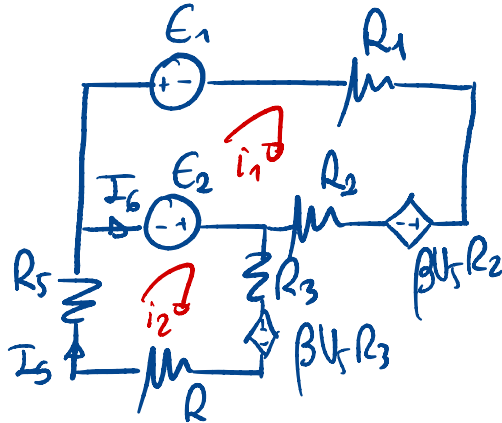

$$i_1 \text{ loop: } -E_1 - \beta U_5 R_2 - E_2 = i_1 (R_1 + R_2) \quad U_5 = i_2 R_5 \rightarrow -E_1 - E_2 = i_1 (R_1 + R_2) + i_2 \beta R_2 R_5$$

$$i_2 \text{ loop: } E_2 - \beta U_5 R_3 = i_2 (R_3 + R_4 + R_5) \quad U_5 = i_2 R_5 \rightarrow E_2 = i_2 (R_3 (1 + \beta R_5) + R_4 + R_5)$$

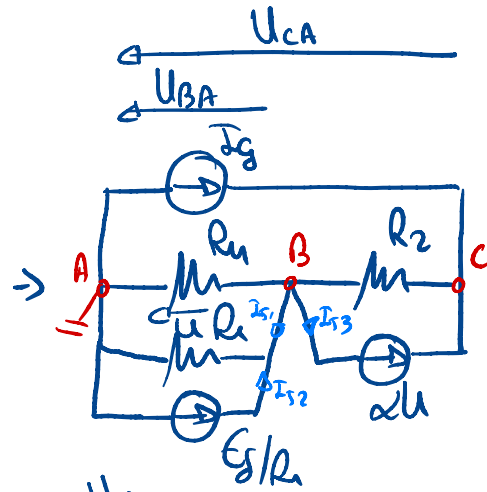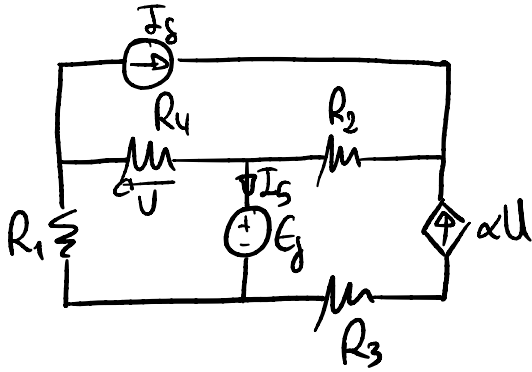Problema 2. I_S , nodos $\diamond \propto U_n$



$$B. \frac{E_S}{R_1} - \alpha U = U_{BA} \left(\frac{1}{R_1} + \frac{1}{R_1} + \frac{1}{R_2} \right) - U_{CA} \frac{1}{R_2} \xrightarrow{U=U_{BA}} \frac{E_S}{R_1} = U_{BA} \left(\alpha + \frac{1}{R_1} + \frac{1}{R_1} + \frac{1}{R_2} \right) - U_{CA} \frac{1}{R_2}$$

$$C. \alpha U + I_S = U_{CA} \frac{1}{R_2} - U_{BA} \frac{1}{R_2} \xrightarrow{U=U_{BA}} I_S = U_{BA} \left(-\frac{1}{R_2} - \alpha \right) + U_{CA} \frac{1}{R_2}$$

$$\hat{i}_S = Y_m \hat{e}_S \rightarrow \begin{pmatrix} \frac{E_S}{R_1} \\ I_S \end{pmatrix} = \begin{pmatrix} \alpha + \frac{1}{R_1} + \frac{1}{R_1} + \frac{1}{R_2} & -\frac{1}{R_2} \\ -\frac{1}{R_2} - \alpha & \frac{1}{R_2} \end{pmatrix} \begin{pmatrix} U_{BA} \\ U_{CA} \end{pmatrix}$$



$$U_{BA} = \frac{\begin{vmatrix} \frac{E_S}{R_1} & -\frac{1}{R_2} \\ I_S & \frac{1}{R_2} \end{vmatrix}}{\begin{vmatrix} \alpha + \frac{1}{R_1} + \frac{1}{R_1} + \frac{1}{R_2} & -\frac{1}{R_2} \\ -\frac{1}{R_2} - \alpha & \frac{1}{R_2} \end{vmatrix}} = \frac{\frac{E_S}{R_1} + \frac{I_S}{R_2}}{\left(\alpha + \frac{1}{R_1} + \frac{1}{R_1} + \frac{1}{R_2} \right) \left(\frac{1}{R_2} \right) - \frac{1}{R_2} \left(\frac{1}{R_2} + \alpha \right)} =$$

$$= \frac{\frac{E_S}{R_1} + I_S}{\frac{1}{R_1} + \frac{1}{R_1}} = \frac{(E_S + I_S R_1) R_1}{R_1 + R_1}$$

$$I_S = I_{S1} + I_{S3} - I_{S2} = \frac{U_{BA}}{R_1} + \alpha U_{BA} - \frac{E_S}{R_1} = U_{BA} \left(\frac{1}{R_1} + \alpha \right) - \frac{E_S}{R_1} =$$

$$= \frac{(E_S + I_S R_1) R_1}{R_1 + R_1} \left(\frac{1}{R_1} + \alpha \right) - \frac{E_S}{R_1}$$

Problema 2. Añadido αU_1

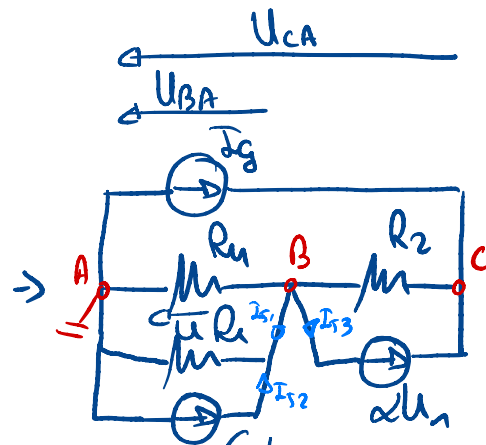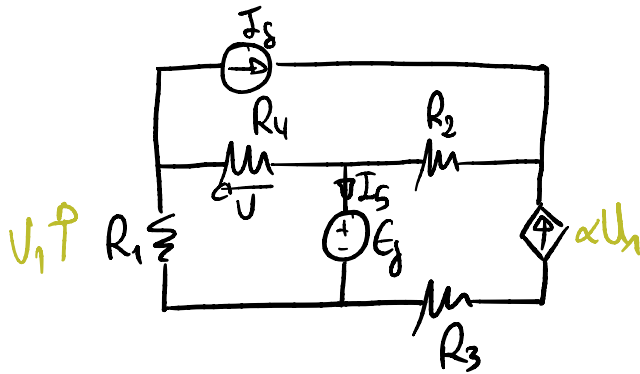


B. $\frac{E_s}{R_2} - \alpha U_1 = U_{BA} \left(\frac{1}{R_4} + \frac{1}{R_1} + \frac{1}{R_2} \right) - U_{CA} \frac{1}{R_2} \rightarrow E_s \left(\frac{1}{R_1} + \alpha \right) = U_{BA} \left(\alpha + \frac{1}{R_4} + \frac{1}{R_1} + \frac{1}{R_2} \right) - U_{CA} \frac{1}{R_2}$

C. $\alpha U_1 + I_s = U_{CA} \frac{1}{R_2} - U_{BA} \frac{1}{R_2} \rightarrow I_s - \alpha E_s = U_{BA} \left(-\frac{1}{R_2} - \alpha \right) + U_{CA} \frac{1}{R_2}$


$$\vec{i}_s = Y_n \vec{e}_s = \begin{pmatrix} \alpha + \frac{1}{R_4} + \frac{1}{R_1} + \frac{1}{R_2} & -\frac{1}{R_2} \\ -\left(\frac{1}{R_2} + \alpha\right) & \frac{1}{R_2} \end{pmatrix} \begin{pmatrix} \frac{E_s}{R_1} + \alpha \\ I_s - \alpha E_s \end{pmatrix}$$

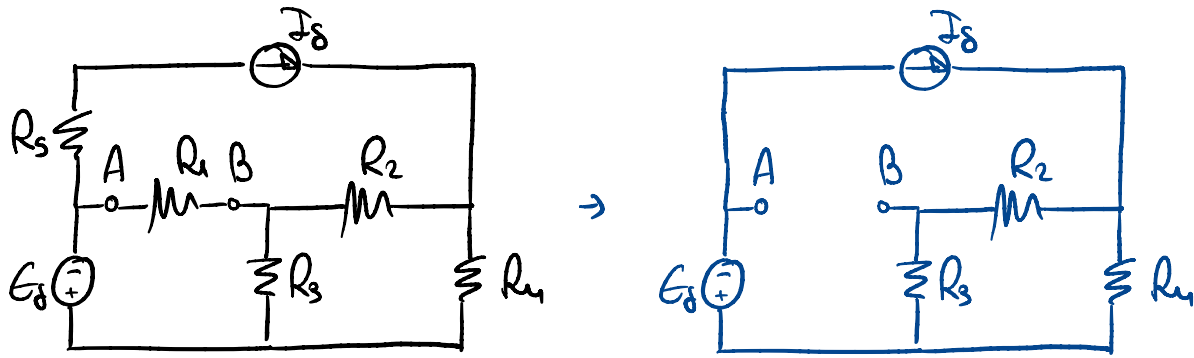Problema 3. Thevenin, Norton

frente tensión independiente \rightarrow circuito abierto
 fuente intensidad independiente \rightarrow cortocircuito



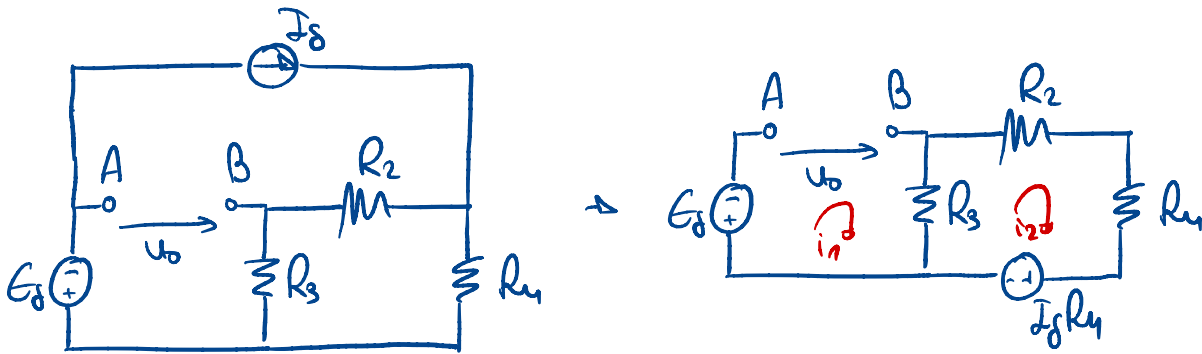- Tensión a circuito abierto U_0 ? $I_0 = 0$




$$i_1 \quad -E_s = i_1 R_3 - i_2 R_3 \xrightarrow{i_1=0} -E_s = -i_2 R_3$$

$$i_2 \quad -I_s R_4 = i_2 (R_2 + R_3 + R_4) - i_1 R_3 \xrightarrow{i_1=0} -I_s R_4 = i_2 (R_2 + R_3 + R_4)$$

$$i_2 = \frac{-I_s R_4}{R_2 + R_3 + R_4}$$

$$U_0 = +i_2 R_3 - E_s = \frac{-I_s R_4 R_3}{R_2 + R_3 + R_4} - E_s = \frac{-E_s (R_2 + R_3 + R_4) - I_s R_4 R_3}{R_2 + R_3 + R_4}$$

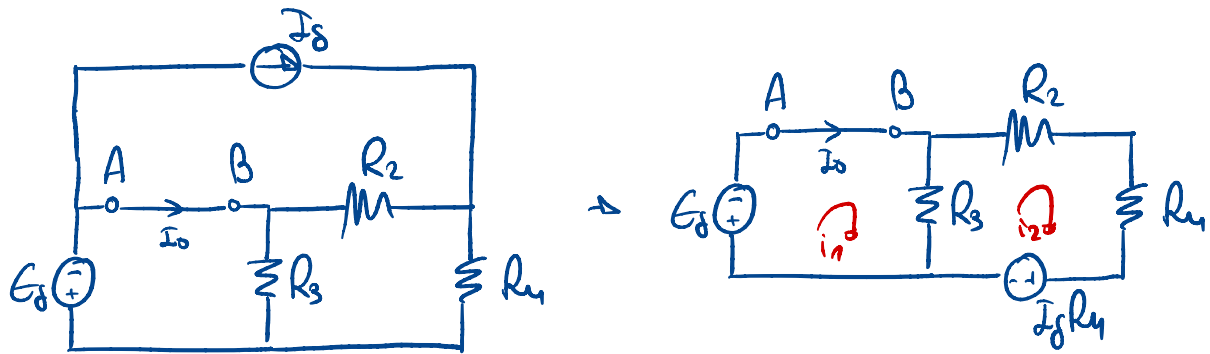- Intensidad de cortocircuito I_0 ? $U_0 = 0$



$$i_1 - E_s = i_1 R_3 - i_2 R_3$$


$$i_2 - I_s R_4 = i_2 (R_2 + R_3 + R_4) - i_1 R_3$$

$$i_1 = \frac{\begin{vmatrix} -E_s & -R_3 \\ -I_s R_4 & R_2 + R_3 + R_4 \end{vmatrix}}{\begin{vmatrix} R_3 & -R_3 \\ -R_3 & R_2 + R_3 + R_4 \end{vmatrix}} = \frac{-E_s (R_2 + R_3 + R_4) - I_s R_4 R_3}{R_3 (R_2 + R_3 + R_4) - R_3^2} =$$

$$= \frac{-E_s (R_2 + R_3 + R_4) - I_s R_4 R_3}{R_3 (R_2 + R_4)} = I_0$$


- Resistencia equivalente R_{eq} ?
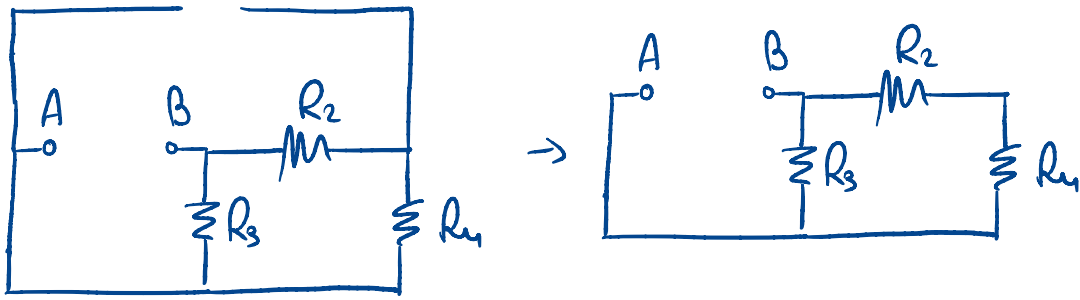
$$R_{eq} = \frac{U_0}{I_0} = \frac{\frac{-E_s (R_2 + R_3 + R_4) - I_s R_4 R_3}{R_2 + R_3 + R_4}}{\frac{-E_s (R_2 + R_3 + R_4) - I_s R_4 R_3}{R_3 (R_2 + R_4)}} = \frac{R_3 (R_2 + R_4)}{R_2 + R_3 + R_4}$$





$$R_{eq} = \frac{1}{\frac{1}{R_3} + \frac{1}{R_2 + R_4}} = \frac{1}{\frac{R_2 + R_4 + R_3}{R_3(R_2 + R_4)}} = \frac{R_3(R_2 + R_4)}{R_2 + R_4 + R_3}$$

Problema 4 Thevenin, Norton

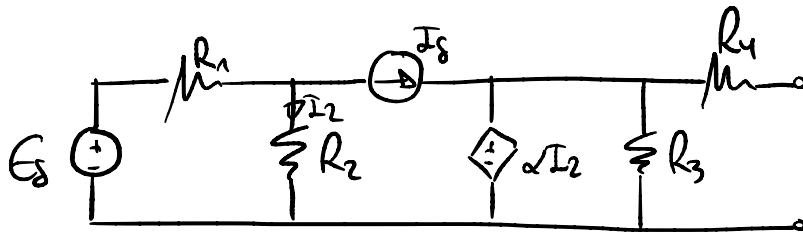

- Tensión circuito abierto U_0 ? $I_0=0$

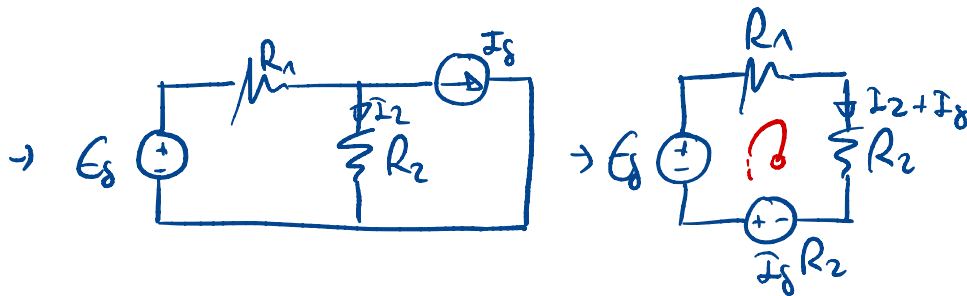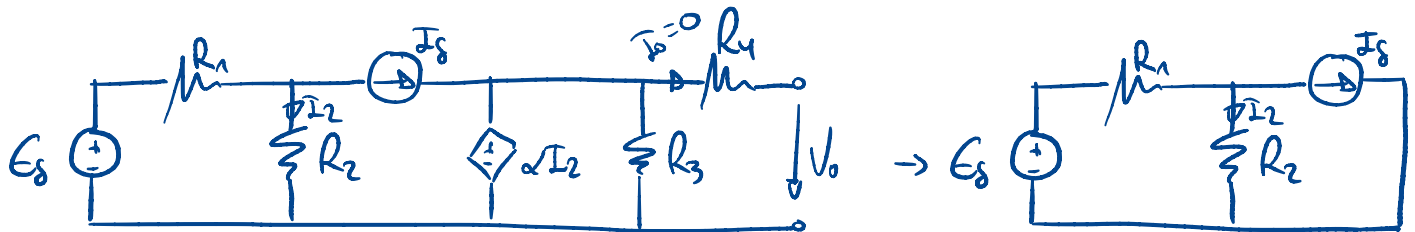




$$E_s + I_2 R_2 = i (R_1 + R_2) \rightarrow i = \frac{E_s + I_2 R_2}{R_1 + R_2}$$

$$i = I_2 + I_2 \rightarrow I_2 = i - I_2 = \frac{E_s + I_2 R_2}{R_1 + R_2} - I_2 = \frac{E_s + I_2 R_2 - I_2 (R_1 + R_2)}{R_1 + R_2} =$$

$$= \frac{E_s - I_2 R_2}{R_1 + R_2}$$

$$U_0 = \alpha \frac{E_s - I_2 R_2}{R_1 + R_2}$$

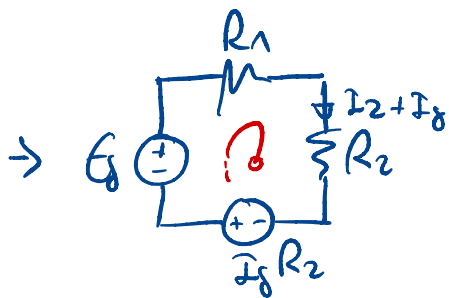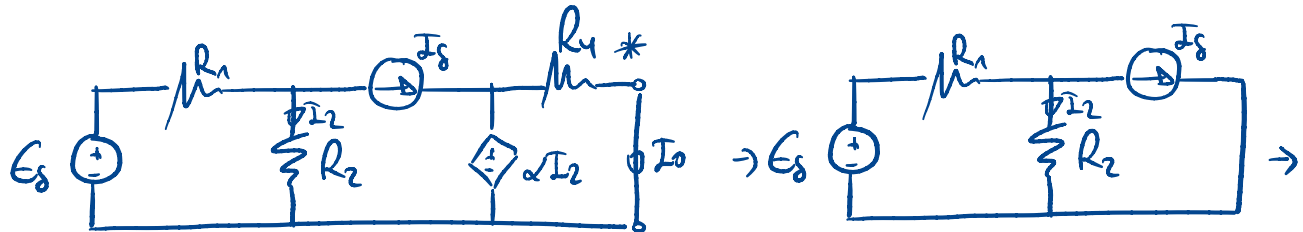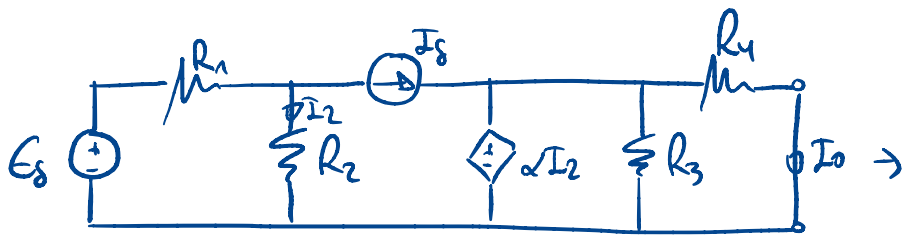- Intensidad cortocircuito I_0 ? $U_0 = 0$





$$E_s + I_s R_2 = i (R_1 + R_2) \rightarrow i = \frac{E_s + I_s R_2}{R_1 + R_2}$$

$$i = I_2 + I_s \rightarrow I_2 = i - I_s = \frac{E_s + I_s R_2}{R_1 + R_2} - I_s = \frac{E_s + I_s R_2 - I_s (R_1 + R_2)}{R_1 + R_2} = \frac{E_s - I_s R_2}{R_1 + R_2}$$

$$* 0 = -\alpha I_2 + R_4 I_0 \rightarrow R_4 I_0 = \alpha I_2 \rightarrow I_0 = \frac{\alpha I_2}{R_4} \left\{ \begin{array}{l} I_0 = \frac{\alpha (E_s - I_s R_2)}{R_4 (R_1 + R_2)} \end{array} \right.$$

- Resistencia equivalente R_{eq} ?
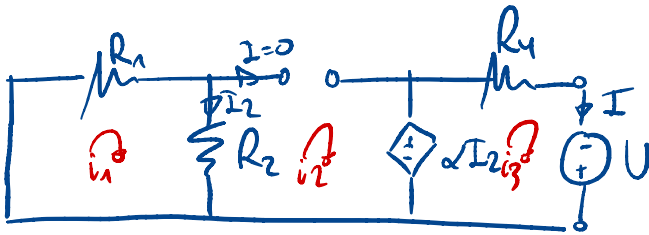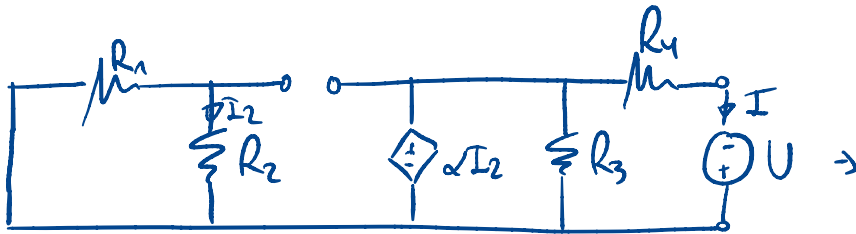
$$R_{eq} = \frac{U_0}{I_0} = \frac{\alpha \frac{E_s - I_s R_2}{R_1 + R_2}}{\frac{\alpha (E_s - I_s R_2)}{R_4 (R_1 + R_2)}} = R_4$$



$$i_1 \circlearrowleft 0 = i_1 (R_1 + R_2) - i_2 R_2 \xrightarrow{I=0} i_1 = 0$$

$$i_2 \circlearrowleft \alpha I_2 = i_2 R_2 - i_1 R_2 \xrightarrow{I=0} I_2 = 0$$

$$i_3 \circlearrowleft U + \alpha I_2 = i_3 R_4 \rightarrow \frac{U}{i_3} = R_4 \rightarrow R_{eq} = R_4$$