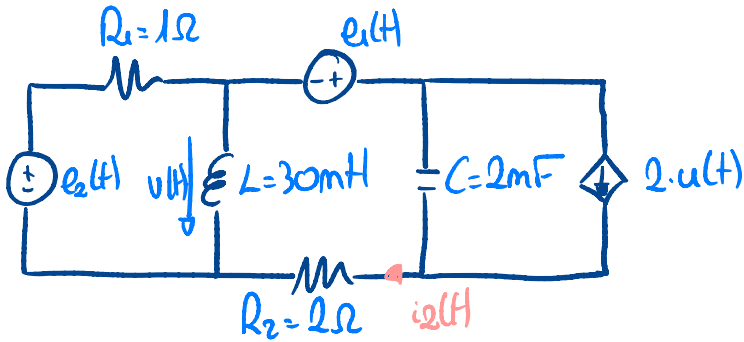


# transformada factorial → senos

Problema 1.  $i_2(t)$  mallas



$$e_1(t) = \sqrt{2} \cdot 150 \cdot \cos(100 \cdot t + \frac{\pi}{4})$$



$$e_2(t) = \sqrt{2} \cdot 100 \cdot \sin(100 \cdot t)$$

$$\omega = 100$$

$$e_1(t) = \sqrt{2} \cdot 150 \cdot \cos(100 \cdot t + \frac{\pi}{4}) = \sqrt{2} \cdot 150 \cdot \sin(100 \cdot t + \frac{\pi}{4} + \frac{\pi}{2}) = \sqrt{2} \cdot 150 \cdot \sin(100 \cdot t + \frac{3\pi}{4})$$


$$Z_L = j \cdot \omega \cdot L = j \cdot 100 \cdot 0.03 = j3$$
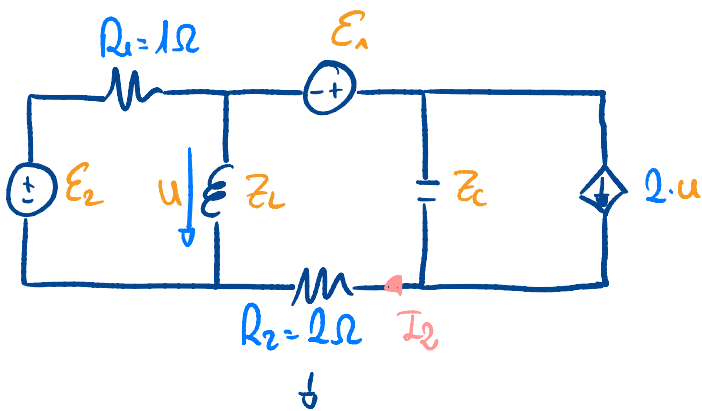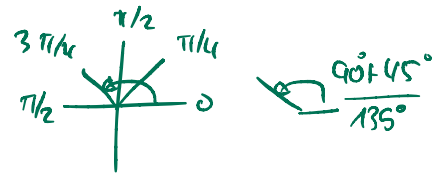
$$Z_C = j \frac{-1}{\omega C} = j \frac{-1}{100 \cdot 2 \cdot 10^{-3}} = -j5$$



$$E_1 = 150 \angle \frac{3\pi}{4} \equiv 150 \angle 135^\circ$$
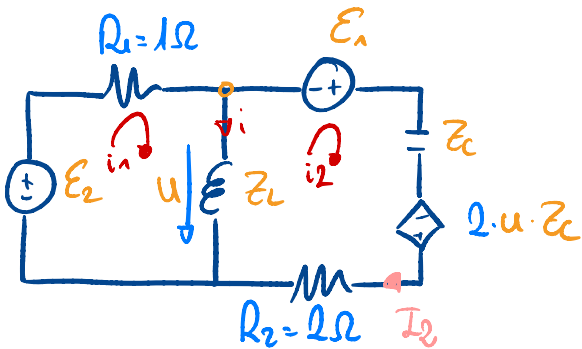
$$E_2 = 100 \angle 0 \equiv 100 \angle 0^\circ$$



$$i_1 \rightarrow \circ \rightarrow i_2 \rightarrow \circ \rightarrow i = i_2 + i_1 \rightarrow i = i_1 - i_2$$

$$\text{Mesh 1: } E_2 = i_1 (R_1 + Z_L) - i_2 Z_L$$

$$\text{Mesh 2: } E_1 + 2 \cdot u \cdot Z_C = i_2 (R_2 + Z_L + Z_C) - i_1 Z_L$$

$$u = i \cdot Z_L \rightarrow u = (i_1 - i_2) Z_L$$

$$E_1 + 2 (i_1 - i_2) Z_L Z_C = i_2 (R_2 + Z_L + Z_C) - i_1 Z_L \rightarrow$$

$$E_1 = i_2 (R_2 + Z_L + Z_C) - i_1 Z_L - 2 (i_1 - i_2) Z_L Z_C \rightarrow$$

$$E_1 = i_2 (R_2 + Z_L + Z_C + 2 Z_L Z_C) - i_1 Z_L (1 + 2 Z_C)$$

# Manteniendo letras

Como  $i_2 = I_2$

$$\text{⌚ } E_2 = i_1 (R_1 + Z_L) - I_2 Z_L$$

$$\text{⌚ } E_1 = -i_1 Z_L (1 + 2Z_C) + I_2 (R_2 + Z_L + Z_C + 2Z_L Z_C)$$

$$I_2 = \frac{\begin{vmatrix} (R_1 + Z_L) & E_2 \\ -Z_L (1 + 2Z_C) & E_1 \end{vmatrix}}{\begin{vmatrix} R_1 + Z_L & -Z_L \\ -Z_L (1 + 2Z_C) & R_2 + Z_L + Z_C + 2Z_L Z_C \end{vmatrix}} =$$

$$= \frac{(R_1 + Z_L)E_1 + E_2 Z_L (1 + 2Z_C)}{(R_1 + Z_L)(R_2 + Z_L + Z_C + 2Z_L Z_C) + Z_L^2 (1 + 2Z_C)}$$

$$= \frac{(1 + j3)150 \angle 45^\circ + 100j3(1 + 2(-j5))}{(1 + j3)(2 + j3 - j5 + 2j3(-j5)) - (j3)^2(1 + 2(-j5))}$$

$$= \frac{(1 + j3)75\sqrt{2} \begin{matrix} \nearrow \text{sen} \\ \searrow \text{cos} \end{matrix} (j-1) + j300(1-j10)}{(1 + j3)(2 - j2 + 30) + 9(1-j10)} = \frac{-j75\sqrt{2} - 75\sqrt{2} - 225\sqrt{2} - j225\sqrt{2} + j300 + 3000}{(1 + j3)(32 - j2) + 9 - j90}$$

$$= \frac{300(10 - \sqrt{2}) + j(300 - 150\sqrt{2})}{32 - j2 + j96 + 6 + 9 - j90} = \frac{300(10 - \sqrt{2}) + j(300 - 150\sqrt{2})}{47 + j4}$$

$$= \frac{2577.23 \angle 1.95^\circ}{47.17 \angle 4.86^\circ} = 54.64 \angle -2.91^\circ$$

$\text{Re}(x, x_j)$

Por lo tanto

$$i_2(t) = \sqrt{2} \cdot 54.64 \cdot \text{sen} \left( \overbrace{100t}^{\omega} - \overbrace{\frac{2.91\pi}{180}}^{a \text{ rad}} \right)$$

# Sustituyendo ASAP

Como  $i_2 = I_2$

$$\textcircled{1} \quad E_2 = i_1 (R_1 + Z_L) - I_2 Z_L$$

$$\textcircled{2} \quad E_1 = -i_1 Z_C (1 + 2Z_C) + I_2 (R_2 + Z_L + Z_C + 2Z_L Z_C)$$

$$\textcircled{1} \quad 100 \angle 0^\circ = i_1 (1 + j3) - I_2 j3 \Rightarrow 100 = i_1 (1 + j3) - I_2 j3$$

$$\begin{aligned} \textcircled{2} \quad 150 \angle 135^\circ &= -i_1 j3 (1 + 2(-j5)) + I_2 (2 + j3 - j5 + 2j3(-j5)) \Rightarrow \\ &\Rightarrow 75\sqrt{2} (j-1) = -i_1 j3 (1 - j10) + I_2 (2 - j2 + j6(-j5)) \Rightarrow \\ &\Rightarrow 75\sqrt{2} (j-1) = -i_1 (j3 + 30) + I_2 (2 - j2 + 30) \Rightarrow 75\sqrt{2} (j-1) = -i_1 3(j+10) + I_2 2(16-j) \end{aligned}$$

$$I_2 = \frac{\begin{vmatrix} 1+j3 & 100 \\ -3(j+10) & 75\sqrt{2}(j-1) \end{vmatrix}}{\begin{vmatrix} 1+j3 & -j3 \\ -3(j+10) & 2(16-j) \end{vmatrix}} = \frac{(1+j3)(75\sqrt{2}(j-1)) + 100 \cdot 3(j+10)}{(1+j3)(2(16-j)) - j3 \cdot 3(j+10)} =$$

$$= \frac{75\sqrt{2}(j-1) + 75\sqrt{2}j3(j-1) + j300 + 3000}{32 - j2 + j96 + 6 + 9 - j90} =$$

$$= \frac{-j75\sqrt{2} - 75\sqrt{2} - 3 \cdot 75\sqrt{2} - j3 \cdot 75\sqrt{2} + j300 + 3000}{47 + j4} =$$

$$= \frac{-j2 \cdot 75\sqrt{2} - 4 \cdot 75\sqrt{2} + j300 + 3000}{47 + j4} = \frac{-300\sqrt{2} + 3000 + j(300 - 150\sqrt{2})}{47 + j4} =$$


$$\begin{aligned} &= \frac{2577.23 \angle 1.95^\circ}{47.17 \angle 4.86^\circ} = 54.64 \angle -2.91^\circ \\ &\uparrow \\ &\text{pol}(x, x_j) \end{aligned}$$

Por lo tanto

$$i_2(t) = \sqrt{2} \cdot 54.64 \cdot \text{sen} \left( \overbrace{100t}^{\omega} - \overbrace{\frac{2.91\pi}{180}}^{a \text{ rad}} \right)$$

$$i_2(t) = 77.27 \text{ sen}(100t - 0.016\pi) = 77.27 \text{ sen}(100t - 0.051)$$

Problema 2.  $i_L(t)$  nodos

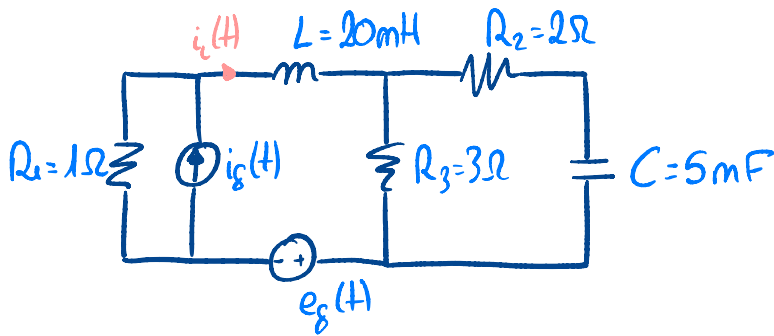

$$e_g(t) = \sqrt{2} 60 \cos(\omega t)$$


$$i_g(t) = \sqrt{2} 10 \sin(\omega t + \frac{\pi}{2})$$

$\omega = 200$

$$e_g(t) = \sqrt{2} 60 \cos(200t) = \sqrt{2} 60 \sin(200t + \frac{\pi}{2})$$

$$Z_L = j \omega L = j 200 \cdot 0.02 = j 4$$



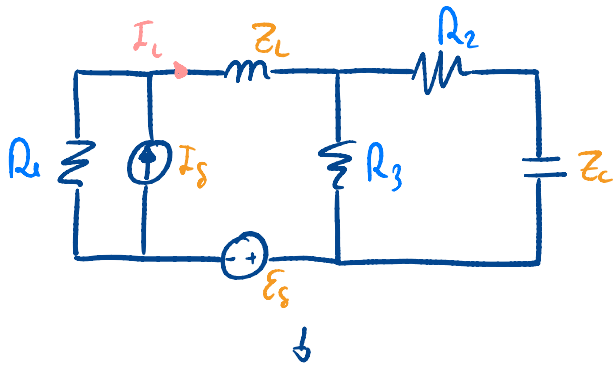
$$Z_C = -j \frac{1}{\omega C} = -j \frac{1}{0.005 \cdot 200} = -j \frac{1}{1} = -j$$



$$I_g = 10 \angle 90^\circ$$

$$E_g = 60 \angle 90^\circ$$

$$Z = Z_C + R_2 = -j + 2$$

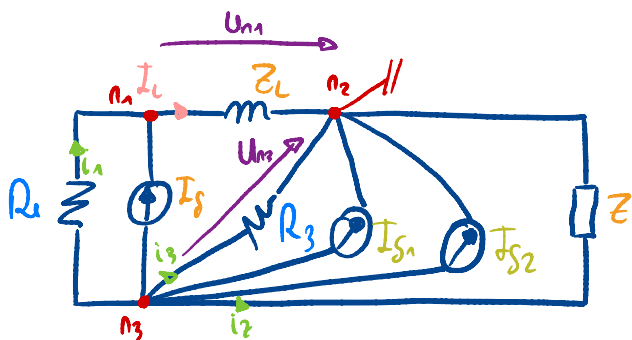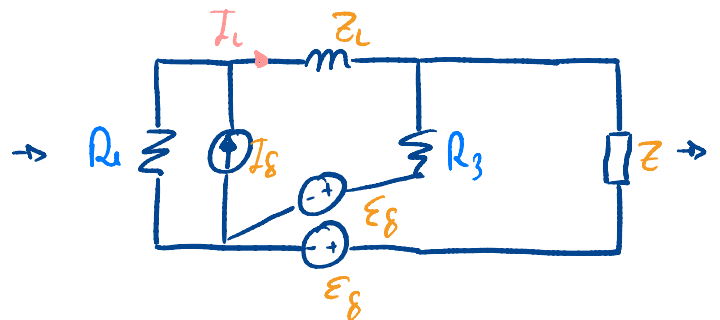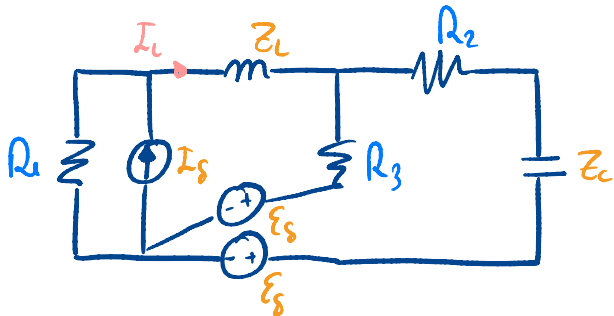

$$I_{S1} = \frac{E_g}{R_3} = \frac{60 \angle 90^\circ}{3} = 20 \angle 90^\circ$$

$$I_{S2} = \frac{E_g}{Z} = \frac{60 \angle 90^\circ}{2-j} = \frac{j 60(2+j)}{(2-j)(2+j)} = \frac{60(j2-1)}{4+j^2-2+1}$$

$$= \frac{60(j2-1)}{5} = 12(j2-1)$$

Manteniendo letras

$$n_1. i_1 + I_S = I_L \rightarrow \frac{(U_{n3} - U_{n1})}{R_1} + I_S = \frac{U_{n1}}{Z_L} \rightarrow I_S = U_{n1} \left( \frac{1}{R_1} + \frac{1}{Z_L} \right) - \frac{U_{n3}}{R_1}$$

$$n_3. 0 = I_1 + I_S + I_3 + I_{S1} + I_{S2} + I_2 \rightarrow 0 = \frac{(U_{n3} - U_{n1})}{R_1} + I_S + I_{S1} + I_{S2} + U_{n3} \left( \frac{1}{R_3} + \frac{1}{Z} \right) \rightarrow$$

$$I_S + I_{S1} + I_{S2} = \frac{U_{n1}}{R_1} - U_{n3} \left( \frac{1}{R_1} + \frac{1}{R_3} + \frac{1}{Z} \right)$$

$$U_{n1} = \frac{\begin{vmatrix} I_S & -\frac{1}{R_1} \\ I_S + I_{S1} + I_{S2} & -\left(\frac{1}{R_1} + \frac{1}{R_3} + \frac{1}{Z}\right) \end{vmatrix}}{\begin{vmatrix} \frac{1}{R_1} + \frac{1}{Z} & -\frac{1}{R_1} \\ \frac{1}{R_1} & -\left(\frac{1}{R_1} + \frac{1}{R_3} + \frac{1}{Z}\right) \end{vmatrix}} =$$

$$= \frac{-I_S \left( \frac{1}{R_1} + \frac{1}{R_3} + \frac{1}{Z} \right) + \frac{1}{R_1} (I_S + I_{S1} + I_{S2})}{-\left(\frac{1}{R_1} + \frac{1}{Z}\right) \left( \frac{1}{R_1} + \frac{1}{R_3} + \frac{1}{Z} \right) + \frac{1}{R_1 Z}} = \frac{I_S \left( \frac{1}{R_1} + \frac{1}{R_3} + \frac{1}{Z} \right) - \frac{1}{R_1} (I_S + I_{S1} + I_{S2})}{\frac{1}{R_1 R_3} + \frac{1}{R_1 Z} + \frac{1}{Z R_1} + \frac{1}{Z R_3} + \frac{1}{Z Z}}$$

$$= \frac{10 \angle 0^\circ \left( \frac{1}{3} + \frac{1}{2-j} \right) - \frac{1}{1} (20 \angle 90^\circ + 12(j2-1))}{\frac{1}{1 \cdot 3} + \frac{1}{1(2-j)} + \frac{1}{j4 \cdot 1} + \frac{1}{j4 \cdot 3} + \frac{1}{j4(2-j)}}$$

$$= \frac{j10 \left( \frac{1}{3} + \frac{2+j}{(2-j)(2+j)} \right) - 1(j20 + j24 - 12)}{\frac{1}{3} + \frac{2+j}{(2-j)(2+j)} + \frac{-j4}{j4(-j4)} + \frac{-j12}{j12(-j12)} + \frac{1}{j8+4}} = \frac{j10 \left( \frac{1}{3} + \frac{2+j}{4+1} \right) - (j44 - 12)}{\frac{1}{3} + \frac{2+j}{4+1} - \frac{j}{4} - \frac{j}{12} + \frac{4-j8}{(j8-4)(4-j8)}}$$

$$= \frac{j10 \left( \frac{1}{3} + \frac{2+j}{5} \right) - j44 + 12}{\frac{1}{3} + \frac{2+j}{5} - \frac{j}{4} - \frac{j}{12} + \frac{4-j8}{64+16}} = \frac{j10 \left( \frac{5+3(2+j)}{15} \right) - j44 + 12}{\frac{80+48(2+j) - j60 - j20 + 3(4-j8)}{240}}$$

$$= \frac{j10 \frac{11+j3}{15} + \frac{-j660+180}{15}}{\frac{80+96+j48-j60-j20+12-j24}{240}} = \frac{j110-30-j660+180}{15} = \frac{-j550+150}{15} = \frac{47-j14}{60}$$

$$= \frac{-j110+30}{47-j14} = \frac{60(-j110+30)}{3(47-j14)} = \frac{20(-j110+30)}{47-j14} = \frac{-j2200+600}{47-j14}$$

$$= \frac{2280.35 \angle -74.74^\circ}{49.04 \angle 16.59^\circ} = 46.50 \angle -58.15^\circ$$

$\rightarrow$   $R(x, x_j)$

Por lo tanto

$$I_L = \frac{U_{n1}}{Z_L} = \frac{46.50 \angle -58.15^\circ}{j4} = \frac{46.50 \angle -58.15^\circ}{4 \angle 90^\circ} = 11.625 \angle -148.15^\circ$$

Por lo tanto

$$i_L(t) = \sqrt{2} |I_L| \sin(\omega t + \alpha(I_L)) = \sqrt{2} \cdot 11.625 \sin(200t - \frac{148.15 \cdot \pi}{180})$$

$$i_L(t) = 16.44 \sin(200t - 0.82\pi) = 16.44 \sin(200t - 2.59)$$

Sustituyendo ASAP

$$n_1. I_S = U_{n1} \left( \frac{1}{R_1} + \frac{1}{Z_L} \right) - \frac{U_{n3}}{R_1} \rightarrow 10 \angle 90^\circ = U_{n1} \left( \frac{1}{1} + \frac{1}{j4} \right) - U_{n3} \frac{1}{1} \rightarrow$$

$$\rightarrow j10 = U_{n1} \left( 1 - \frac{j}{4} \right) - U_{n3} \rightarrow j10 = U_{n1} \left( \frac{4-j}{4} \right) - U_{n3}$$

$$n_2. I_S + I_{S1} + I_{S2} = \frac{U_{n1}}{R_1} - U_{n3} \left( \frac{1}{R_1} + \frac{1}{R_3} + \frac{1}{Z} \right) \rightarrow$$

$$\rightarrow 10 \angle 90^\circ + 20 \angle 90^\circ + 12(j2-1) = U_{n1} \frac{1}{1} - U_{n3} \left( \frac{1}{1} + \frac{1}{3} + \frac{1}{2-j} \right) \rightarrow$$

$$\rightarrow j10 + j20 + j24 - 12 = U_{n1} - U_{n3} \left( 1 + \frac{1}{3} + \frac{2+j}{5} \right) \rightarrow$$

$$\rightarrow j54 - 12 = U_{n1} - U_{n3} \frac{15+5+3(2+j)}{15} \rightarrow j54 - 12 = U_{n1} - U_{n3} \frac{26+j3}{15}$$

$$U_{n1} = \frac{\begin{vmatrix} j10 & -1 \\ j54-12 & -\frac{26+j3}{15} \end{vmatrix}}{\begin{vmatrix} \frac{4-j}{4} & -1 \\ 1 & -\frac{26+j3}{15} \end{vmatrix}} = \frac{-j10 \frac{26+j3}{15} + 1 \cdot (j54-12)}{-\frac{4-j}{4} \frac{26+j3}{15} + 1 \cdot 1} = \frac{-j260+30+15(j54-12)}{-104-j12+j26-3+60} =$$

$$= \frac{4 \cdot (30 - j260 + j810 - 180)}{-47 + j14} = \frac{4(j550 - 150)}{j14 - 47} = \frac{j2200 - 600}{j14 - 47} =$$

$$= \frac{2280.35 \angle 105.26^\circ}{49.04 \angle 163.41^\circ} = 46.50 \angle -58.15^\circ$$

Pol(x, xj)

Por lo tanto

$$I_L = \frac{u_m}{Z_L} = \frac{46.50 \angle -58.15^\circ}{j4} = \frac{46.50 \angle -58.15^\circ}{4 \angle 90^\circ} = 11.625 \angle -148.15^\circ$$

Por lo tanto


$$i_L(t) = \sqrt{2} |I_L| \sin(\omega t + \alpha(I_L)) = \sqrt{2} \cdot 11.625 \sin(\underbrace{200t}_{\omega} - \underbrace{\frac{148.15 \cdot \pi}{180}}_{\alpha \text{ rad}})$$

$$i_L(t) = 16.44 \sin(200t - 0.82\pi) = 16.44 \sin(200t - 2.59)$$

Complejos  $z_1 = 4 - j3$ ;  $z_2 = 3 + j$


Suma

$$z = z_1 + z_2 = 7 - j2$$

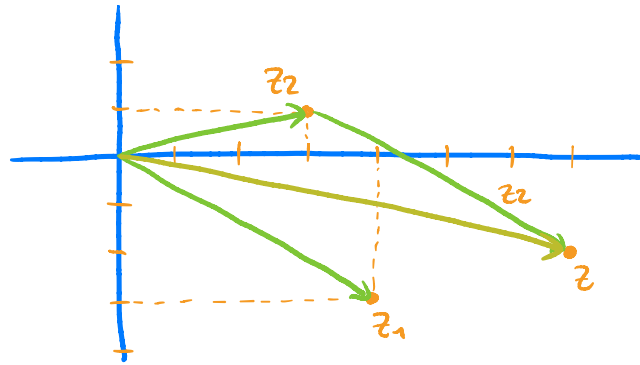

Resta

$$z = z_1 - z_2 = 1 - j4$$

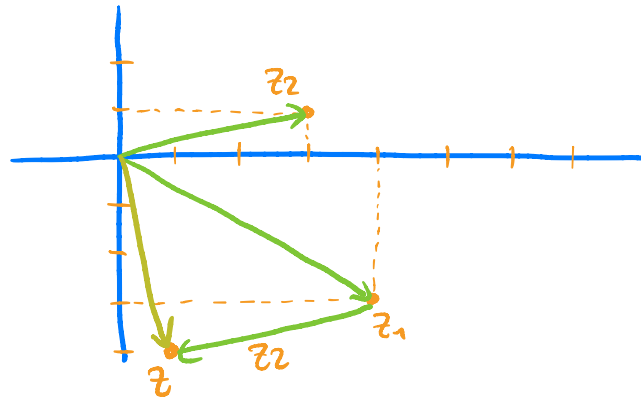


Multiplicación

$$z = z_1 \cdot z_2 = (4 - j3)(3 + j) = 12 + j4 - j9 + 3 = 15 - j5$$

$$\alpha_1 = \text{atg} = \frac{-3}{4} \sim -36.87^\circ \quad |z_1| = \sqrt{4^2 + (-3)^2} = 5$$
$$\alpha_2 = \text{atg} = \frac{1}{3} \sim 18.43^\circ \quad |z_2| = \sqrt{1^2 + 3^2} = \sqrt{10}$$

$$|z_1| \cdot |z_2| = 5 \sqrt{10} \sim 15.81$$
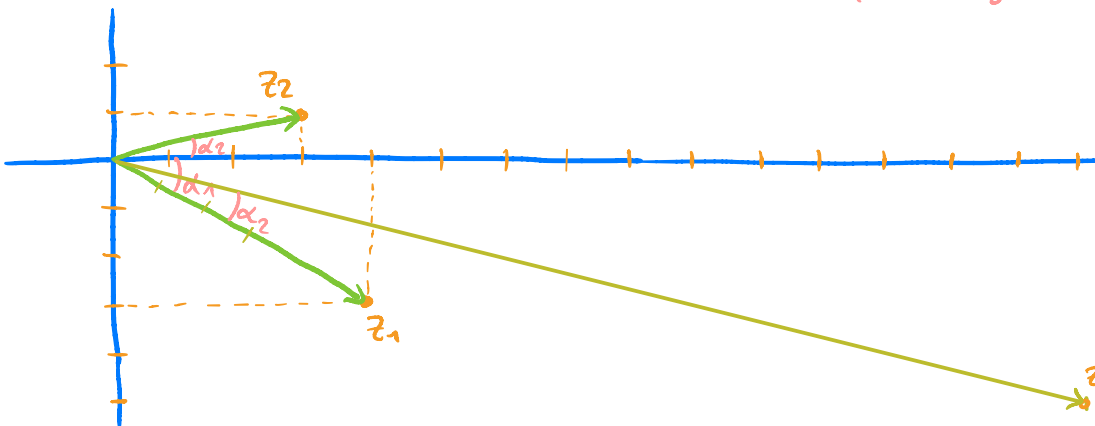
$$\alpha_1 + \alpha_2 = \text{atg} \frac{-3}{4} + \text{atg} \frac{1}{3} \sim -18.43^\circ$$





División

$$z = \frac{z_1}{z_2} = \frac{(4-j3)}{(3+j)} = \frac{(4-j3)(3-j)}{(3+j)(3-j)} =$$

$$\frac{12-j4-j9-3}{9+1} = \frac{9-j13}{10}$$

$$\alpha_1 = \operatorname{atg} = \frac{-3}{4} \sim -36.87^\circ \quad |z_1| = \sqrt{4^2 + (-3)^2} = 5$$

$$\alpha_2 = \operatorname{atg} = \frac{1}{3} \sim 18.43^\circ \quad |z_2| = \sqrt{1^2 + 3^2} = \sqrt{10}$$

$$|z_1|/|z_2| = 5/\sqrt{10} = 5\sqrt{10}/10 = \sqrt{10}/2$$

$$\alpha_1 - \alpha_2 = \operatorname{atg} \frac{-3}{4} - \operatorname{atg} \frac{1}{3} \sim -55.30^\circ$$

